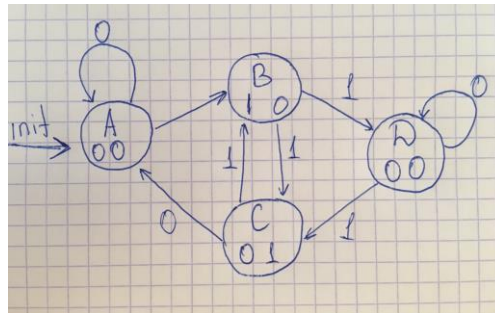


<h1>Digital Circuits Laboratory report</h1>	<h1>Year 2020</h1> <p>Number of the exercise: 2</p>
<p>1. Name and surname (author of realized circuit/this report): Nykonchuk Illia</p> <p>CAD<sup>1</sup></p>	<p><b>Title of the exercise: Synthesis of synchronous circuit</b></p>
<p>Laboratory group number:</p> <p>Breadboard number:</p>	<p>Week day: Thursday</p> <p>Hours of the lab:17:05-18:45</p>


# Moore machine

**Moore machine** is a finite-state machine whose output values are determined only by its current state.

## States-outputs graph



a) Logic Circuit

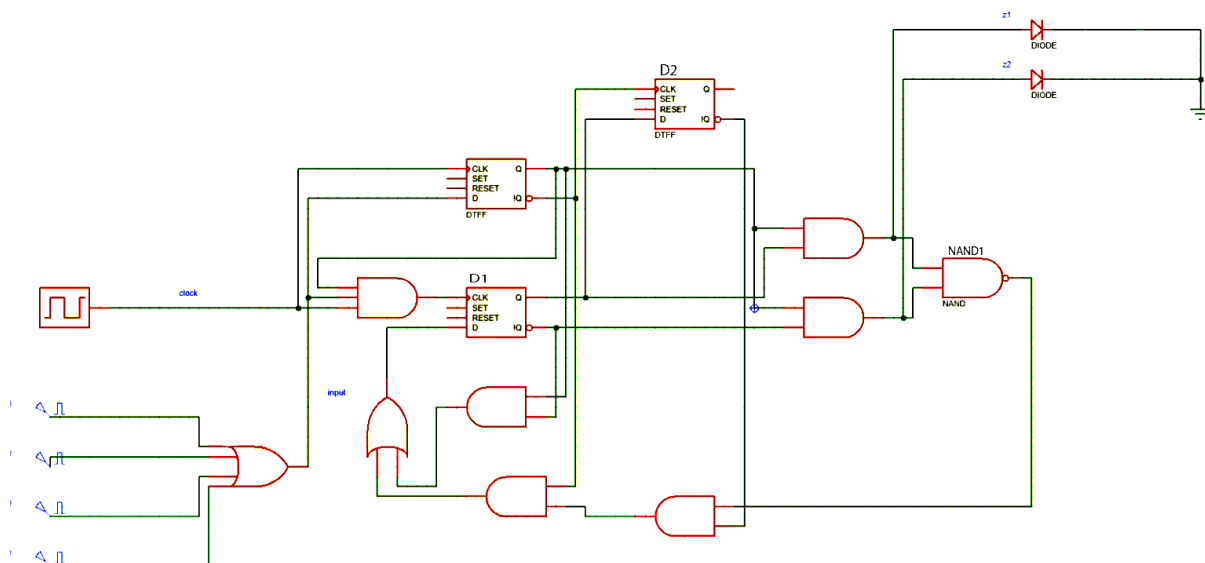

Remark: D2 stores last even value, D1 responsible for output and it resets by the data from output or from D2

## b) Minimization of states-outputs table

Input	$D_1$	$D_2$	NAND1	$Z_1$	$Z_2$
0	x	x	x	0	0
1	x	1	<del>x</del> 1	0	1
1	x	0	1	1	0
1	1	x	0	0	1
1	0	x	0	1	0

Coding of states:

A:  $D_1(Q)=0$ , NAND1 = 1

B:  $D_1(Q)=1$ , NAND1 = 0

C:  $D_1(Q)=0$ , NAND1 = 0

D:  $D_1(Q)=1$ , NAND1 = 1

## c) Excitation tables:

D1

$Q_n$	$Q_{n+1}$	$D_2$
0	0	Never
0	1	0
1	0	1
1	1	Never

D2


$Q_n$	$Q_{n+1}$	X	$D_2$
x	0	↓	0
x	1	↓	1
0	0	↑	x
1	1	↑	x

D3


$Q_n$	$Q_{n+1}$	X
0	0	0
0	1	1
1	0	0
1	1	1

**Mealy Machines** are also finite state machines with output value and its output depends on present state and current input symbol

States-outputs graph:

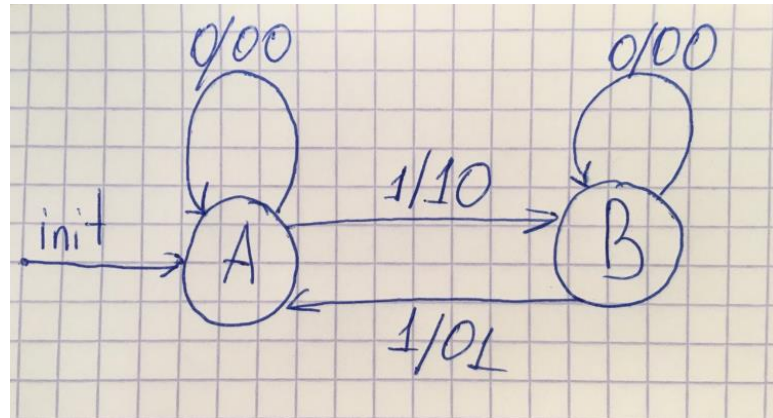

Logic circuit

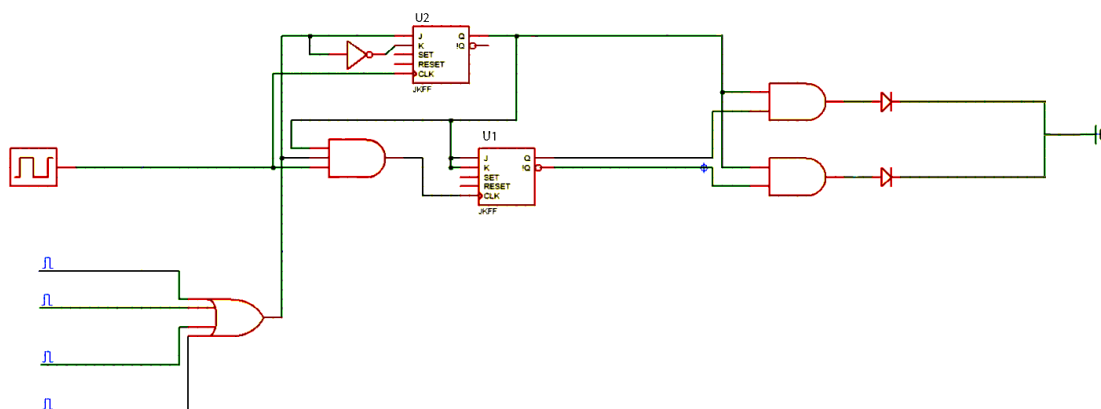

Minimized states-outputs table

X	Q	!Q	Z <sub>1</sub>	Z <sub>2</sub>
1	1	0	0	1
0	0	1	1	0
0	x	x	0	0

Coding of states:

A:  $U1(Q)=1, U1(!Q)=0$ ;

B:  $U1(Q)=1, U1(!Q)=1$ ;

Excitation tables: (U1 and U2 are on the circuit)


U1 flip-flop

$Q_n$	$Q_{n+1}$	$U_2(Q)$
0	0	0
1	1	0
1	0	1
0	1	1

U2 flip-flop

$Q_n$	$Q_{n+1}$	X
x	1	1
x	0	0

Time diagram for sequence 1111000000

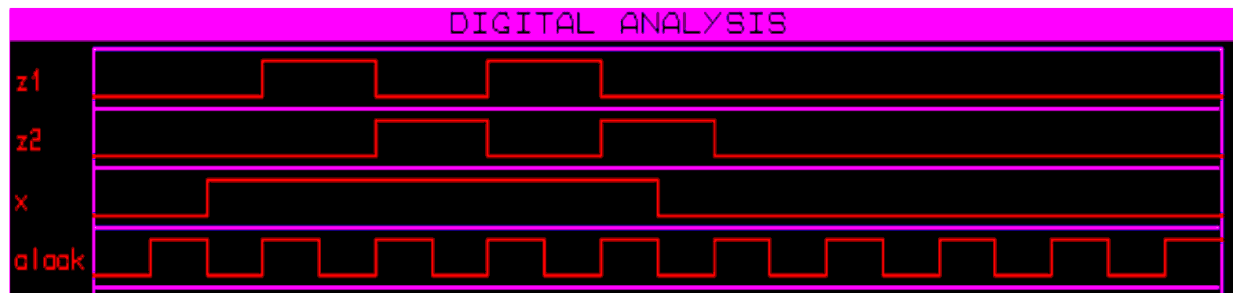

Time diagram for sequence 0000001111

